



# Autonomous Systems

## Exercise 1

1. Write the numbers in Binary, Gray, Hexadecimal, Octa, and Quaternary code (Base 4).

59, 71, 21, 98, 44, 33, 50, 19, 5, 32, 204, 504, 256, 124.

2. How many bits do we need in order to represent:

- All the elements of the sets  $\{-71, -70, \dots, 23, 24\}$  and  $\{3n + 1 : -5 < n < 11, n \in \mathbb{N}\}$ .
- 9 Unique Symbols. 17 Unique Symbols. 60 Unique Symbols. 1325 Unique Symbols.

3. Simplify the following functions:

$$F_1(X, Y) = X\bar{Y} + Y.$$

$$F_2(X, Y, Z) = X \cdot Z + Y \cdot (\bar{X} \cdot Z + \bar{Y}).$$


$$F_3(A, B, C) = B \cdot (A \cdot B + A \cdot \bar{B}) \cdot (\bar{A} \cdot \bar{C} + C).$$

$$F_4(A, B, C, D) = \overline{(C + A \cdot B \cdot \bar{C} + \bar{B} \cdot \bar{C} \cdot D)} + \overline{(C + (\bar{C} \cdot B + \bar{D}))}.$$

$$F_5(X, Y, Z, W) = W \cdot X \cdot Y \cdot Z + W \cdot X \cdot Y \cdot \bar{Z} + W \cdot X \cdot \bar{Y} \cdot Z + W \cdot X \cdot \bar{Y} \cdot \bar{Z} \\ + \bar{W} \cdot X \cdot Y \cdot \bar{Z} + W \cdot \bar{X} \cdot Y \cdot \bar{Z} + \bar{W} \cdot \bar{X} \cdot \bar{Y} \cdot \bar{Z} + \bar{W} \cdot X \cdot \bar{Y} \cdot Z.$$

## Exercise 2

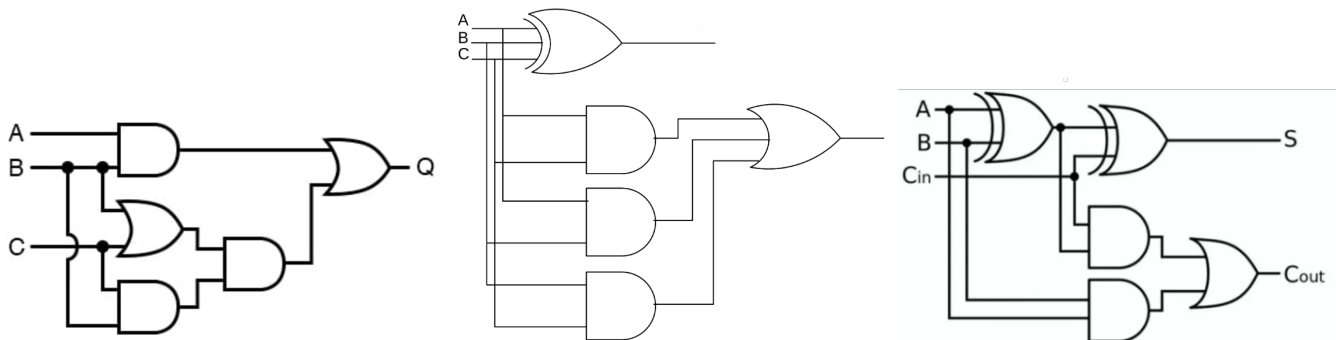1. Turn each of the circuits into boolean expressions.



2. Find the algebraic function of the following truth tables using 3 methods.

| $A$ | $B$ | $C$ | $F$ |
|-----|-----|-----|-----|
| 0   | 0   | 0   | 0   |
| 0   | 0   | 1   | 1   |
| 0   | 1   | 0   | 0   |
| 0   | 1   | 1   | 1   |
| 1   | 0   | 0   | 1   |
| 1   | 0   | 1   | 1   |
| 1   | 1   | 0   | 1   |
| 1   | 1   | 1   | 1   |

| $x$ | $y$ | $z$ | $F$ |
|-----|-----|-----|-----|
| 0   | 0   | 0   | 0   |
| 0   | 0   | 1   | 1   |
| 0   | 1   | 0   | 0   |
| 0   | 1   | 1   | 0   |
| 1   | 0   | 0   | 1   |
| 1   | 0   | 1   | 1   |
| 1   | 1   | 0   | 1   |
| 1   | 1   | 1   | 1   |

| $A$ | $B$ | $C$ | $F$ |
|-----|-----|-----|-----|
| 0   | 0   | 0   | 1   |
| 0   | 0   | 1   | 0   |
| 0   | 1   | 0   | 0   |
| 0   | 1   | 1   | 1   |
| 1   | 0   | 0   | 1   |
| 1   | 0   | 1   | 0   |
| 1   | 1   | 0   | 1   |
| 1   | 1   | 1   | 0   |

## Exercise 3

- A 4-bit binary number is represented as  $A_3A_2A_1A_0$ , where  $A_0$  is the LSB. Design a logic circuit that will produce a HIGH output whenever the binary number is greater than 0010 and less than 1000.
- Design a combinatorial circuit that detects the parity of a 4-bits sequence coded on the inputs  $A, B, C$  and  $D$ . The output  $F(A, B, C, D)$  is equal to 0 if the number of 1's is even and 1 otherwise.
- Design the combinational circuit that converts a 3-bit binary number to its gray code.

## Bonus Question

Examine the sequential circuit below. First, give a complete truth table, then describe conceptually what the circuit does.

